

ME 362

Instrumentation and Measurement Sessional

Home Task-1

Date of Submission: 12 November, 2016 (sec: A)
14 November, 2016 (sec: C)
15 November, 2016 (sec: B)

1. Design a circuit using BD135 transistor in Breadboard that can drive a simple DC motor in clockwise and anticlockwise direction. Use LDR as on/off switch.
2. Design a circuit using BD135 transistor in Breadboard that can drive a simple DC motor in clockwise and anticlockwise direction. Use one or two LDR to change the direction of the motor. (OPTIONAL)